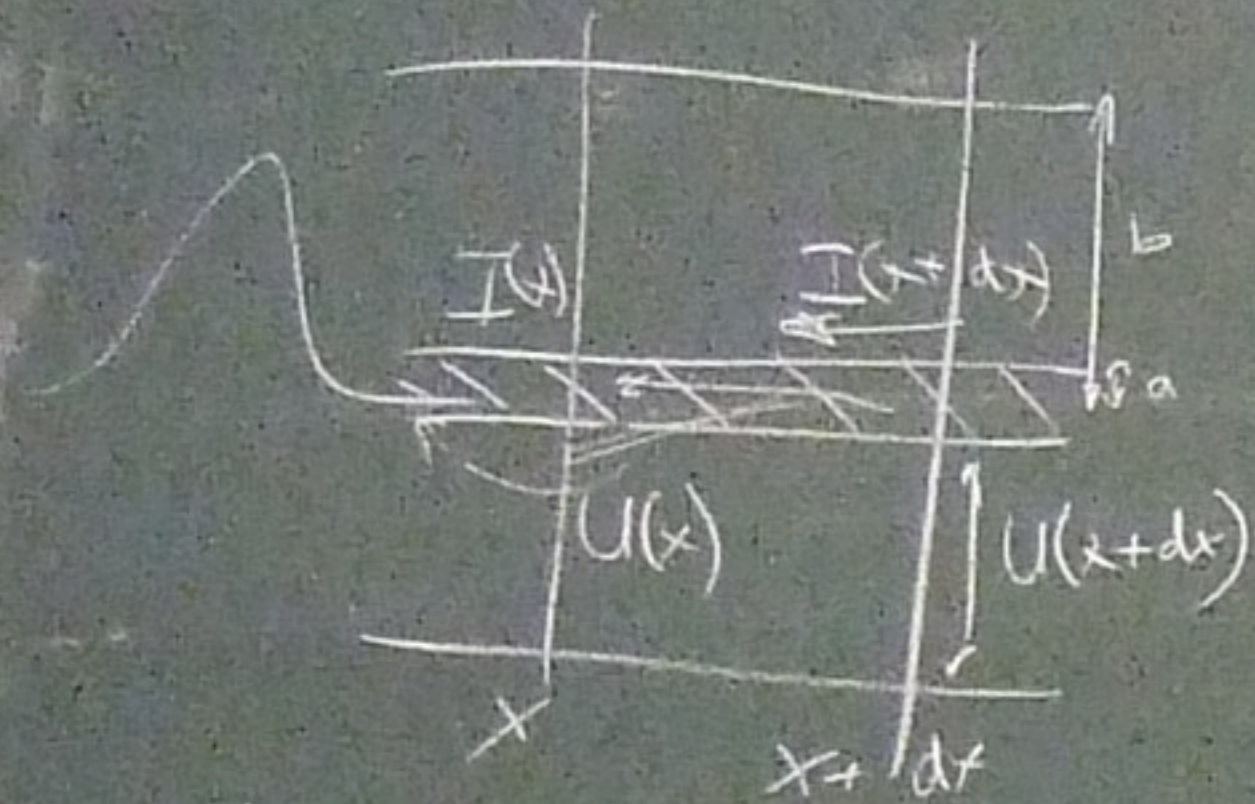


Nachtrag



$$dU = -L dx \frac{\partial I}{\partial t} \quad (\text{Ind.}) \quad \vec{B}' = \frac{I'}{r}$$

$$-dI = +C dx \frac{\partial U}{\partial t} \quad (\text{Kond.}) \quad \vec{E} = U \frac{\partial I}{\partial x} = -C \frac{\partial U}{\partial t}$$

$$U \sim \sin(\omega t - kx)$$


$$I \sim \cos(\omega t - kx)$$

$$\frac{\partial I}{\partial x} \sim -\cos(\omega t - kx)$$


$$I \sim \sin(\omega t - kx)$$

I ~ U Phasenof Ausbreitung

Elektromagnetische Wellen in Hohlleitern

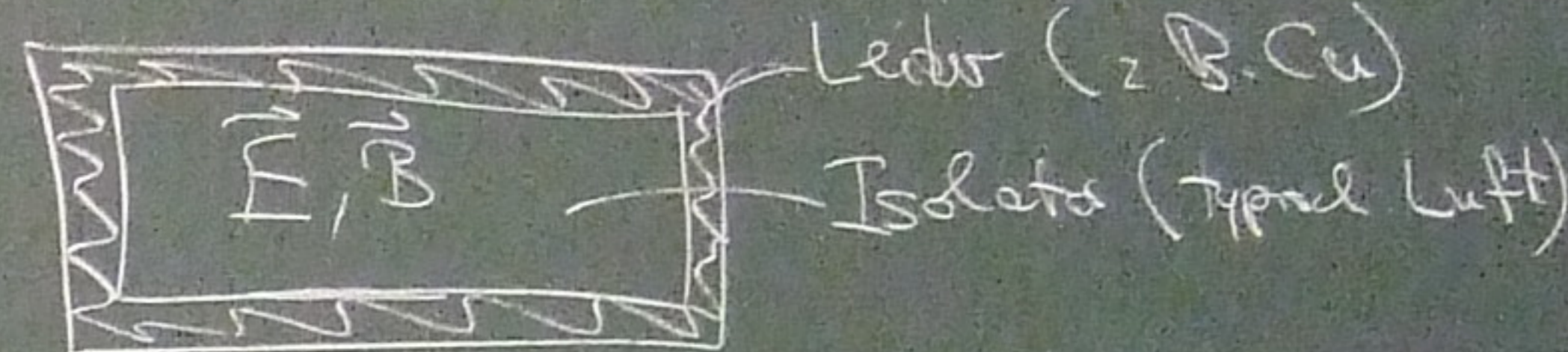

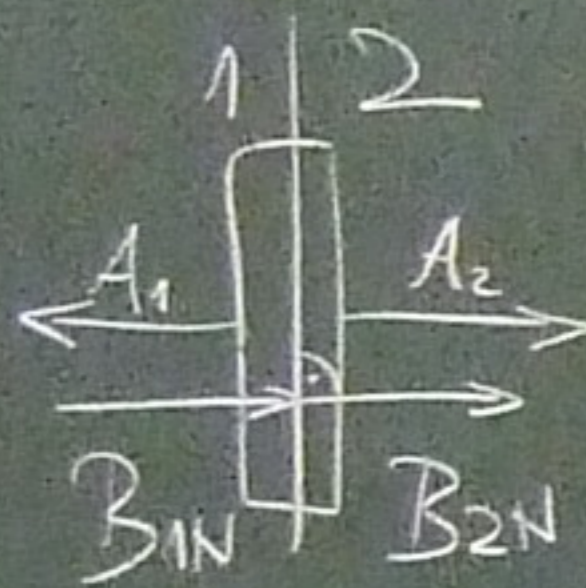Wegen $\text{div } \vec{B} = 0 \rightarrow \Delta B_{\text{Normal}} = 0$




aus $B_{\text{Leiter}} = 0$ (Leiter)

$\rightarrow B_{\text{Luft}} = 0$

$$\frac{B_{1T}}{\mu_1} - \frac{B_{2T}}{\mu_2} = \mu_0 \frac{N}{L} I$$

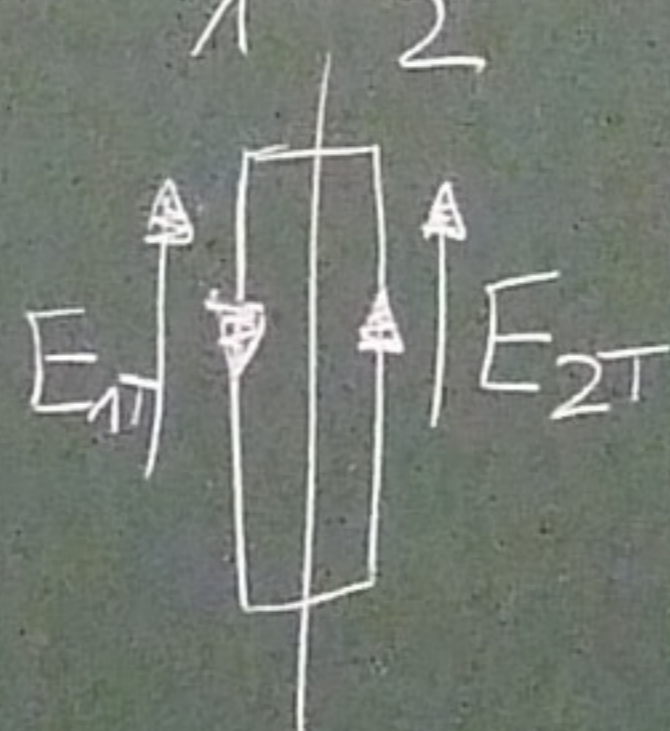Wegen $\text{rot } \vec{E} = -\dot{\vec{B}} \rightarrow \Delta E_{\text{Tangential}} = 0$




aus $E_{\text{Leiter}} = 0$

$\rightarrow E_{\text{Luft}} = 0$

$$\epsilon_1 E_{1N} - \epsilon_2 E_{2N} = \frac{\sigma}{\epsilon_0}$$





← Ladungsflächendichte

Transversal-Elektrische Welle

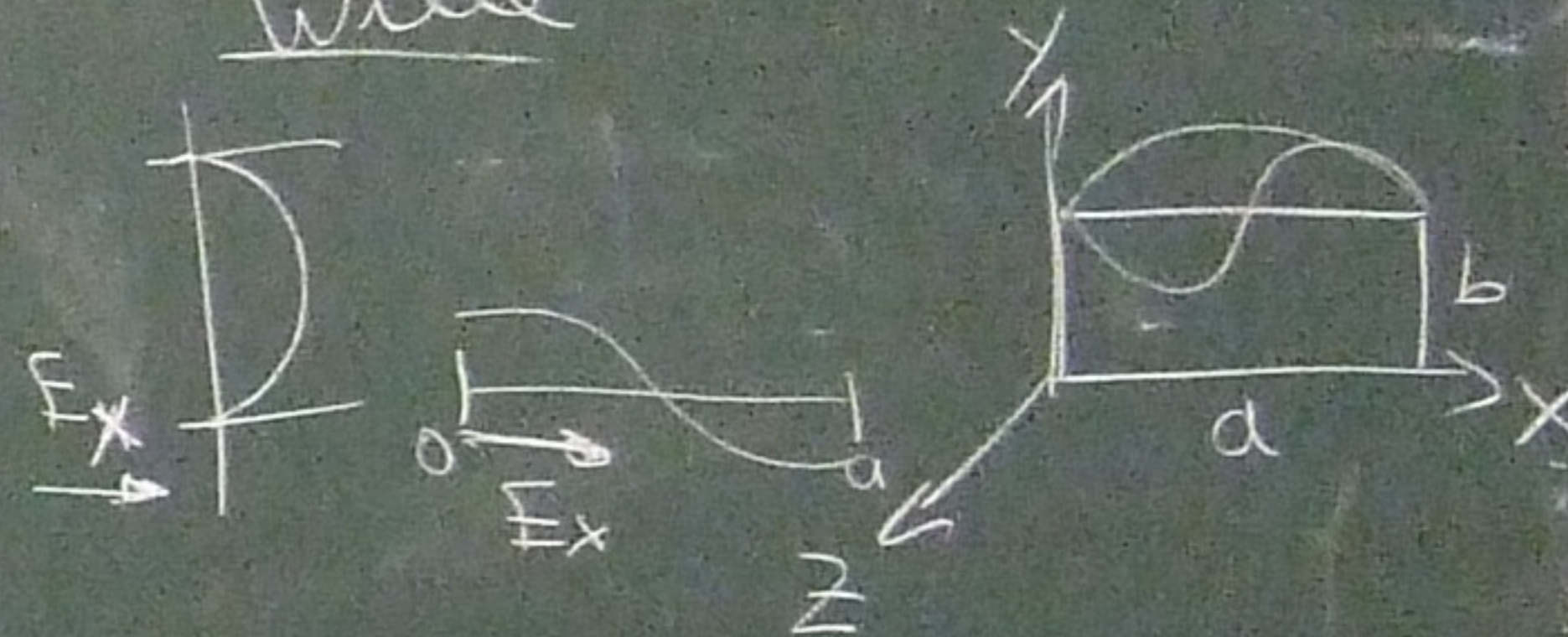

$$E_x = -\frac{m E_0}{b} \cos\left(\frac{n\pi}{a} x\right) \sin\left(\frac{m\pi}{b} y\right) \sin(\omega t - kz)$$
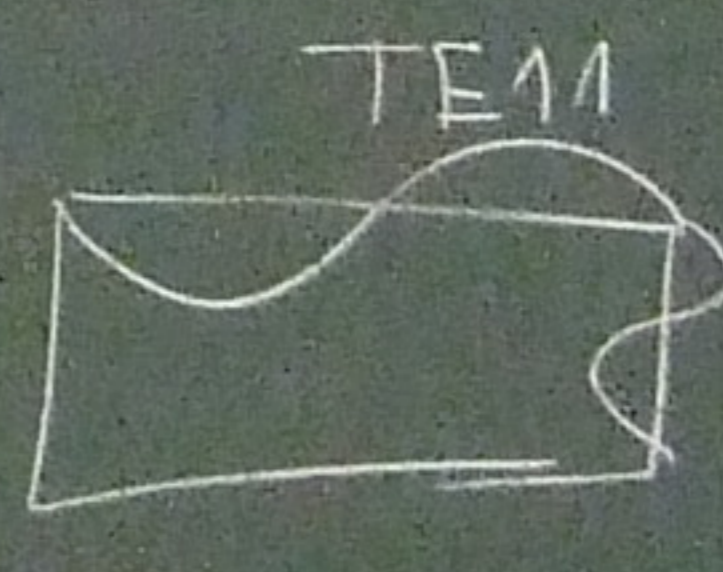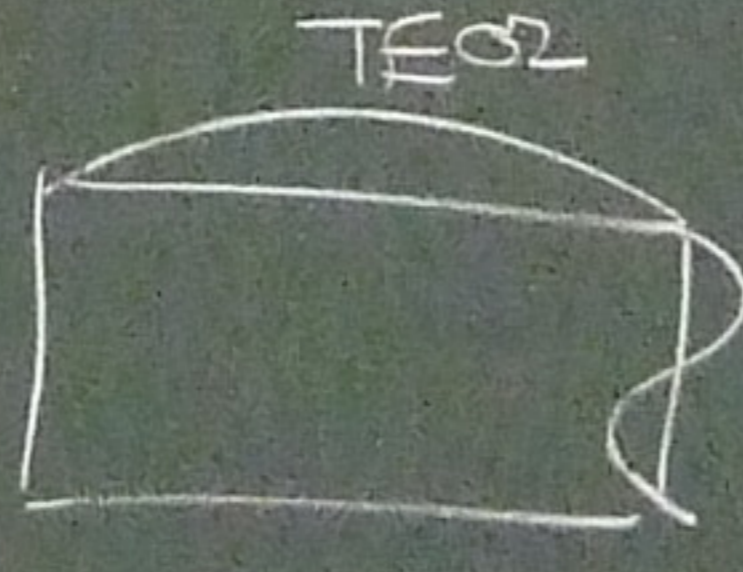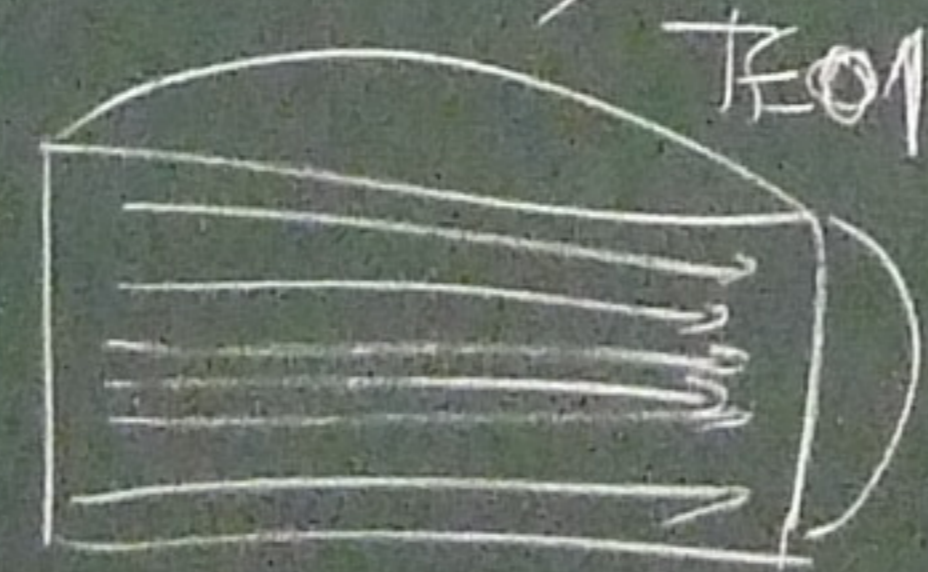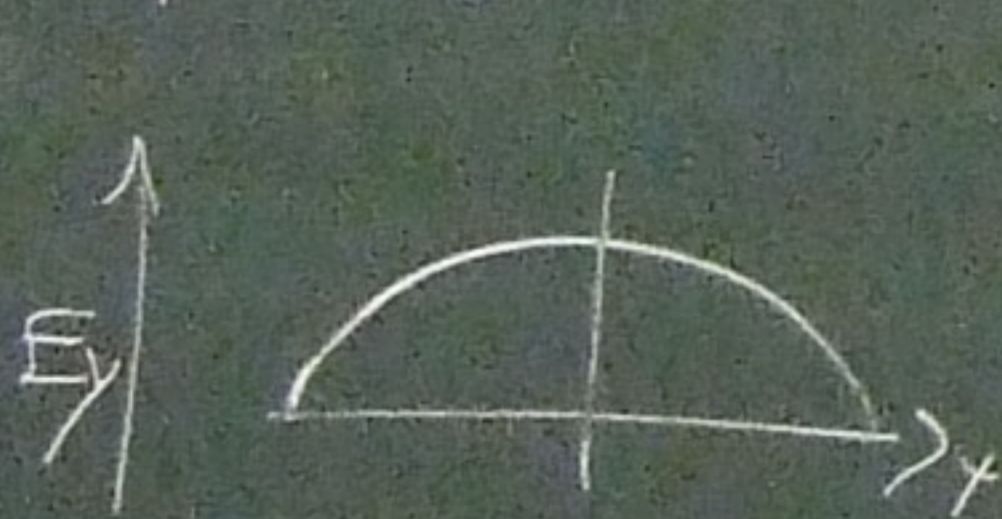
$$E_y = \frac{n E_0}{a} \sin\left(\frac{n\pi}{a} x\right) \cos\left(\frac{m\pi}{b} y\right) \sin(\omega t - kz)$$



∃ Grenzfrequenz $\omega_G = c \sqrt{\left(\frac{m\pi}{b}\right)^2 + \left(\frac{n\pi}{a}\right)^2}$


Die Wellengleichung wird erfüllt, falls

$$\Delta \vec{E} = -\frac{1}{c^2} \ddot{\vec{E}}$$

mit $n=0,1$
 $m=0,1$

$$\frac{\omega^2}{c^2} = k^2 + \left(\frac{m\pi}{b}\right)^2 + \left(\frac{n\pi}{a}\right)^2$$


Aufladen & Entladen eines Kondensators

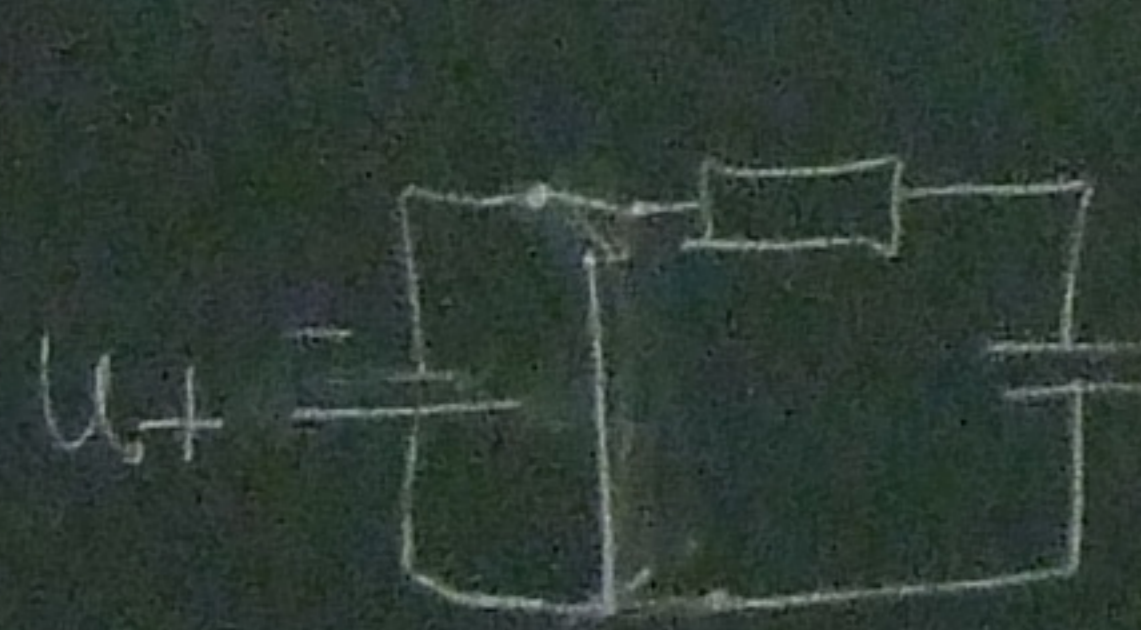

$$\begin{cases} U_0 \\ 0 \end{cases} = U_c + IR \quad \tau = RC$$

$$0 = U_c + RC \dot{U}_c = U_c + \tau \dot{U}_c$$


Kondensator: $I = \dot{Q} = C \dot{U}$

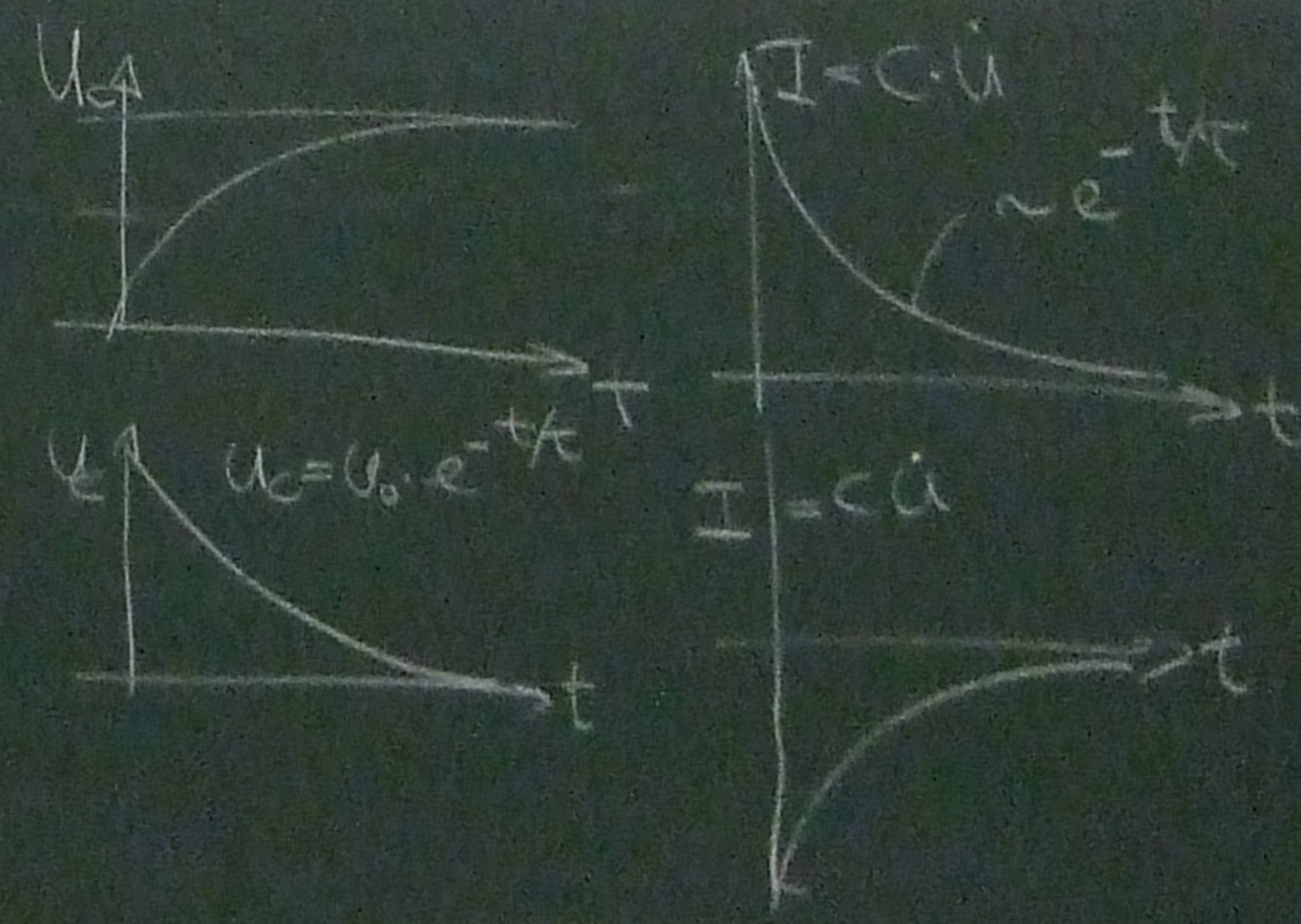

$C = 79 \mu F$
 $R = 20 k\Omega$
 $\tau = 1,6 s$


Übergang zur komplexen Schreibweise

z.B. Reihenschwingkreis. Lösung $I_1 = \hat{I}_1 e^{-\frac{R}{2L}t} \cos(\omega t + \varphi)$
 Genauso gut zweite Lösung: $I_2 = \hat{I}_2 e^{-\frac{R}{2L}t} \sin(\omega t + \varphi)$

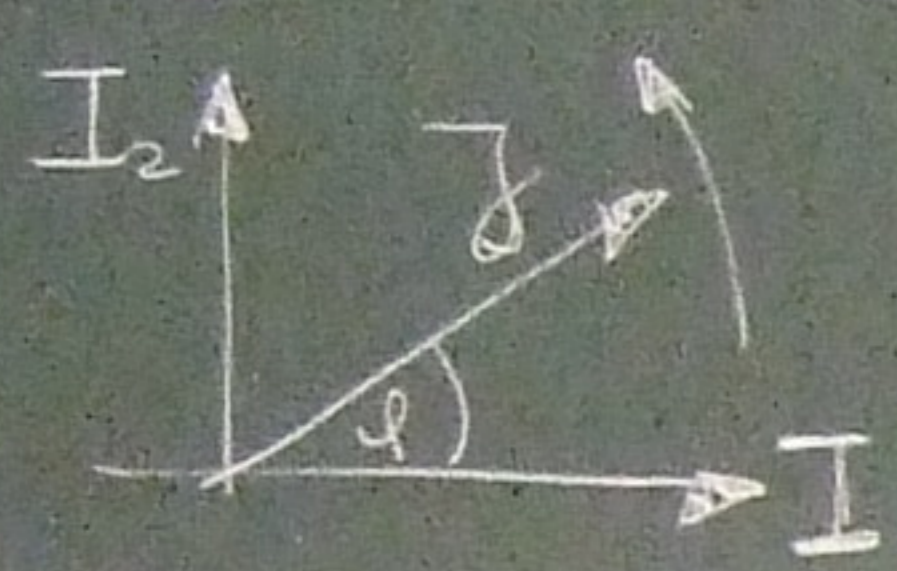I_2  $I = I_1 + i I_2 = \hat{I} e^{-\frac{R}{2L}t} e^{i(\omega t + \varphi)}$
 Physikalische Sachverhalt: $\text{Re}(I)$ oder $\text{Im}(I)$


Für die Diff- & Integration gilt

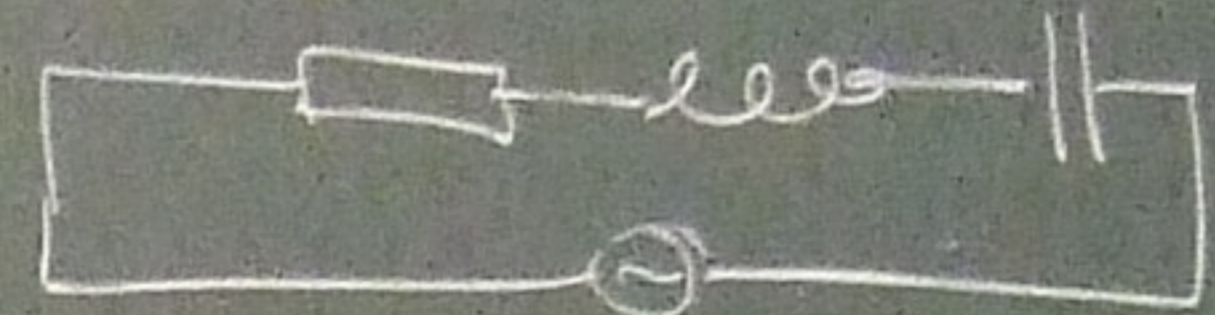
$\frac{d}{dt} I = i\omega I \quad \int I dt = \frac{1}{i\omega} I$



$U = \hat{U} e^{i\omega t} = R \cdot I + L \dot{I} + \frac{1}{C} \int I dt$
 $= R I + i\omega L I + \frac{1}{i\omega C} I$

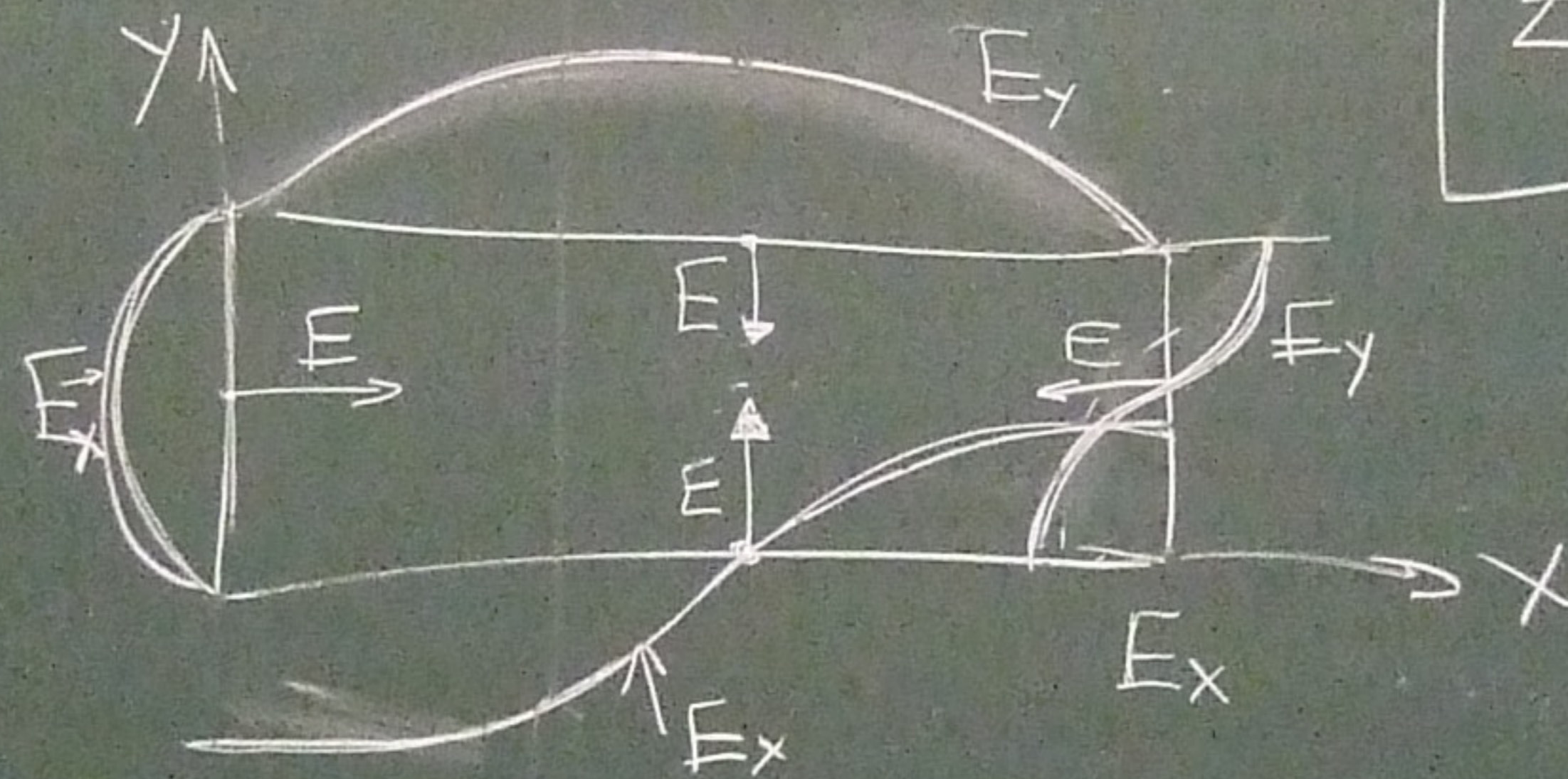$E_x \sim \cos(x) \sin(y)$
 $E_y \sim \sin(x) \cos(y)$



$Z = \frac{U}{I} = \left(R + i\omega L + \frac{1}{i\omega C} \right) |Z|$
 $E_T = 0$  $\tan \varphi = \frac{\text{Im } Z}{\text{Re } Z}$

 $Z = R + i\omega L$

I Den Wechselstromwiderstand

